SystemC and Electronic System Level Design Methodology

Assignment 3, 2024-03-18


Abstract

Implement a half-adder. Then use two (2) half-adders to implement a full adder.

Please read carefully. All outputs required are described in the text. Five (5) points will be taken for each bug, missing required output and behavior.

The half-adder SC_METHOD module Description_


1. A half-adder schematic is given below

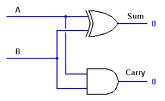

- 2. Use above schematic as the specification and implement a SC_MODULE with a SC_METHOD process, for which the module must be named as HalfAdder. All input and output ports must be named exactly the same as in the schematic.
- 3. You must name the SystemC files as HalfAdder.h and HalfAdder.cpp. This is to make it easier to compile your code using my makefile. Fail to do so will be penalized with 5 pts.

The full-adder SC_METHOD module Description

1. A full-adder schematic is given below

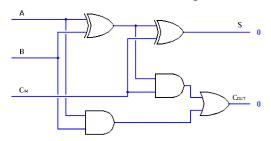

2. Use above schematic as the specification and implement a SC_MODULE with a SC_METHOD process, for which the module must be

named as FullAdder. You must instantiate two (2) half-adders developed above to implement this full-adder. Again, all input and output ports are named exactly the same as in the schematic. C_{in} should be named as Cin and C_{out} should be named as Cout.

3. You must name the SystemC files as FullAdder.h and FullAdder.cpp. Fail to do so will be penalized with 5 pts.

sc main

<u>Description</u>

- 1. Create two test suites in one sc_main, and you must name the file main.cpp, that
 - Instantiate both half-adder and full-adder modules
 - Provide all possible combinations to these modules, i.e. 4 input vectors to the half-adder and 8 input vectors to the full-adder.
- 2. Create a trace file named RESULT. vcd. And trace ports are shown as follows:
 - ▶ Half-adder A
 - ▶ Half-adder B
 - ▶ Half-adder Sum
 - ▶ Half-adder Carry
 - ▶ Full-adder A
 - ▶ Full-adder B
 - ▶ Full-adder Cin
 - ▶ Full-adder s
 - ▶ Full-adder Cout

makefile

Description

 A makefile must be provided, with proper modifications to your environment.

<u>Please</u> turn in the source codes and makefile only. Combine all the files using zip, gzip, or tar. Please do not use rar. Do not turn in the executable.

Due date

2:00 PM, March 25, 2024

Score weight (towards the final grade) 5%